

PROJECT REPORT

“Demonstrate the working of frequency -selective circuit in a single input and has two LED's at the output.LED-1 will be turned ON if input signal frequency is greater than 2kHz. LED-2 will be ON, if input signal is 6kHz.”

TEAM

NAME	USN
S R VAMSHITH	NNM22EC137
S VAISHALI PAI	NNM22EC138
SAHANA PRABHU	NNM22EC139
G PRAWJAL SHETTY	NNM23EC508
OMKAR V PATTAR	NNM23EC514
BALAMURUGAN	NNM23EC506

CIRCUIT DESIGN:

- The Resistor voltages are

$$R1=Q/Wo*C*Af=270k \text{ ohm}$$

$$R2=Q/Wo*C(AQ^2-Af)=340 \text{ ohm}$$

$$R3=2Q/Wo*C=150k \text{ ohm}$$

- Assuming quality factor $Q=500$

- The gain can be computed as

$$Af= Ao= R3/2R1=1$$


- The capacitor values are

$$C1=0.01\mu F$$

$$C2=0.93Nf$$


- $Wo=2*\pi*f$

CIRCUIT SCHEMATIC:

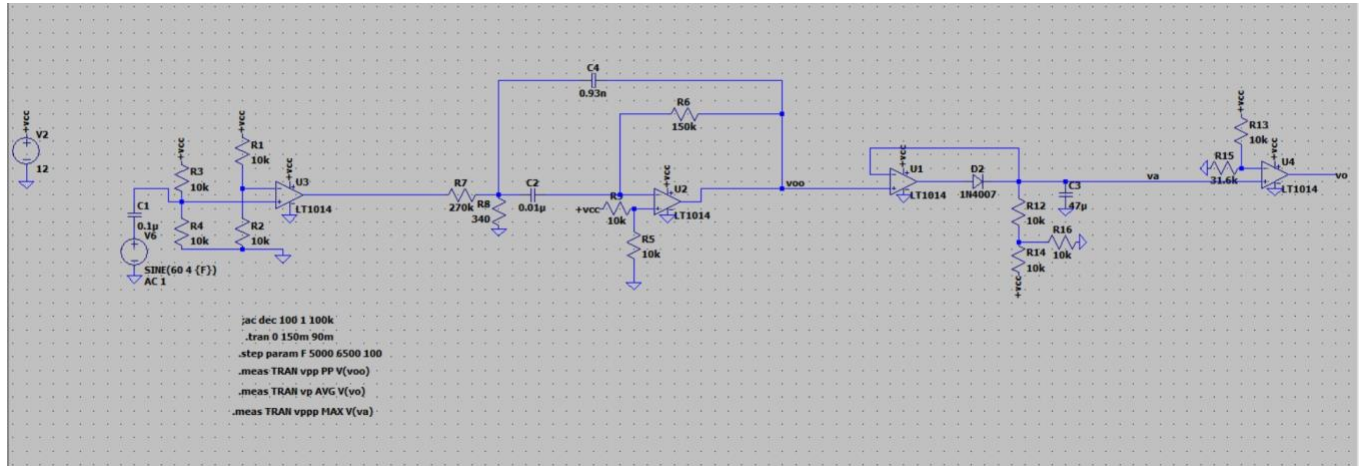

WAVEFORMS:

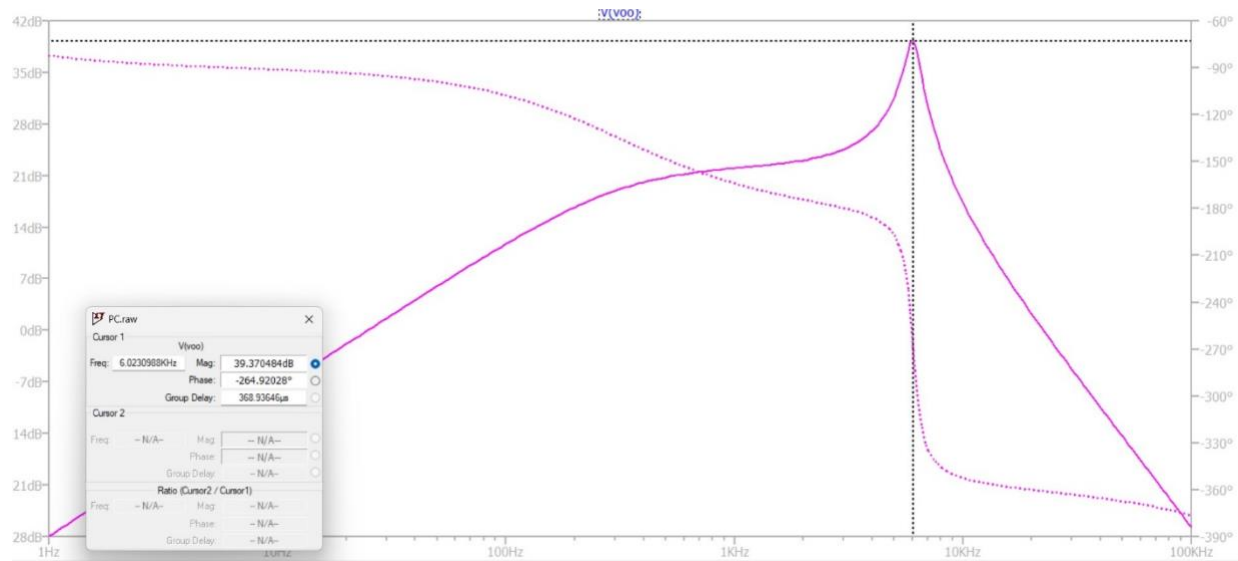output waveform of narrow band filter (voo):



```

.step f=5000
.step f=5100
.step f=5200
.step f=5300
.step f=5400
.step f=5500
.step f=5600
.step f=5700
.step f=5800
.step f=5900
.step f=6000
.step f=6100
.step f=6200
.step f=6300
.step f=6400
.step f=6500

```

```

Measurement: vp
step      AVG(v(vo))
1         0.0142541
2         0.0142541
3         0.0142541
4         0.0142541
5         0.0142541
6         0.0142541
7         0.0142541
8         0.0142541
9         0.014265
10        0.0232784
11        11.3341
12        0.0172203
13        0.0142564
14        0.0142541
15        0.0142541
16        0.0142541

```

INFERENCE:

A frequency-selective circuit was implemented and verified, featuring a LEDs at the output. One LED illuminates when the input signal is at 6 kHz, providing a clear indication of the circuit's frequency-selective behavior.

CIRCUIT DESIGN:

- The frequency of the circuit


$$F_h = 1/2 \cdot \pi \cdot R \cdot C$$

- $\omega = 2 \cdot \pi \cdot F_h$
- Resistor value $R_1 = 8k \text{ ohm}$ And $R_2 = 8k \text{ ohm}$
- The capacitor values are

$$C_1 = 0.01 \mu\text{F}$$


$$C_2 = 0.01 \mu\text{F}$$

CIRCUIT SCHEMATIC:

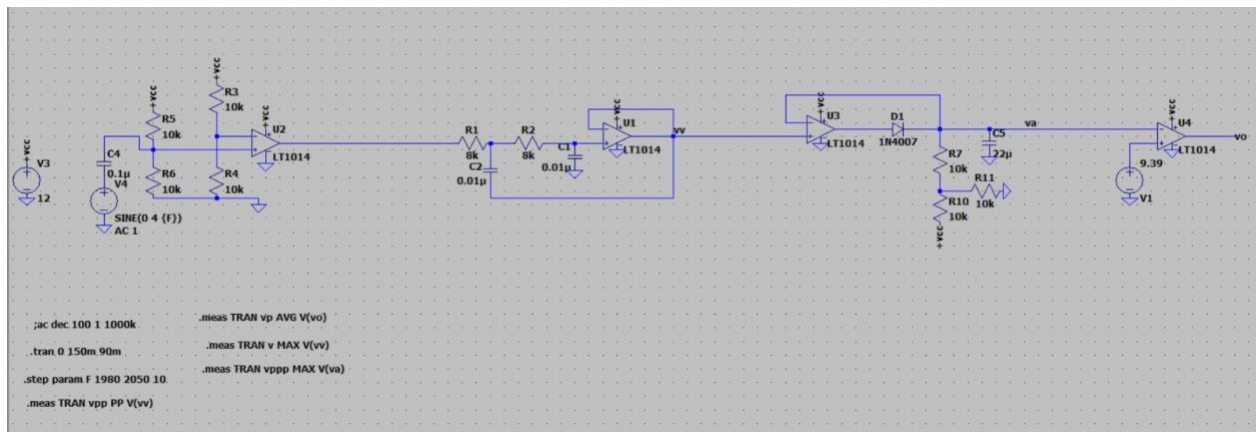

WAVEFORMS:

output waveform of filter :

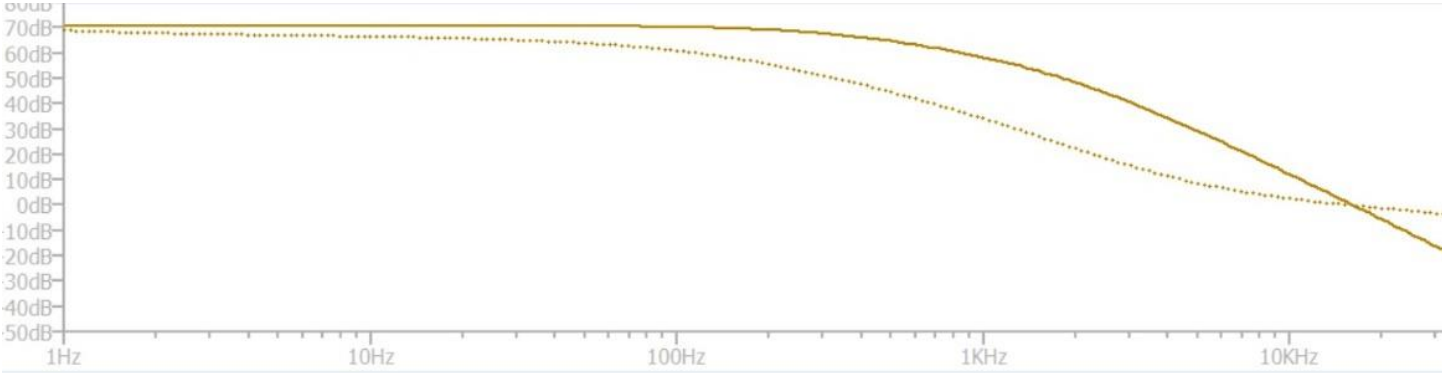

```
.step f=1980
.step f=1990
.step f=2000
.step f=2010
.step f=2020
.step f=2030
.step f=2040
.step f=2050
```

Measurement: vp

step	AVG (v (vo))
1	0.0395031
2	0.0706227
3	11.3419
4	11.3748
5	11.3942
6	11.4049
7	11.4111
8	11.4143

INFERENCE:

A frequency-selective circuit was implemented and verified, featuring a LEDs at the output. One LED illuminates when the input signal is at greater than 2kHz, providing a clear indication of the circuit's frequency-selective behavior

PCB DESIGN :

